

# CURRENT ELECTRICITY ..

Hints:

- ✓ it is a mechanism whereby charges flow from one point to another within a circuit

## ELECTRIC CURRENT (I)

- ✓ Is the rate of flow of electric charges
- ✓ It is measured in Ammeter

Mathematically

Electric current = Quantity of charges  
unit time

$$I = \frac{Q}{t}$$

- ✓ The SI-unit of electric current is Ampere (A)

## AMPERE

- ✓ Is the current flowing through a point in a conductor when a charge of one coulomb passes through a point after every one second

Hints

$$1 \text{ Ampere} = \frac{1 \text{ coulomb}}{1 \text{ second}}$$

## QUANTITY OF CHARGE

- ✓ Is the energy that is transferred from one point to another within a conductor carrying current in a circuit
- The SI-unit is coulomb.

## Coulomb (C)

Is the charge that is transported by constant current of one ampere in one second.

OR

Is the quantity of electricity passing at a given point in one second when a steady current of one Ampere (A) is flowing in a circuit

Hints:

$$1 \text{ coulomb} = 1 \text{ Ampere} \times 1 \text{ second}$$

$$1 \text{ C} = 1 \text{ A} \times 1 \text{ s}$$

- Device that is used to measure electric current is AMMETER
- The other units of electric current are millampere (mA), kiloampere (KA), microampere (μA)

## EQUIVALENCE

$$1 \text{ A} = 10^3 \text{ mA}$$

$$1 \text{ A} = 10^6 \mu\text{A}$$

$$1 \text{ KA} = 10^3 \text{ A}$$

## ELECTRIC POTENTIAL DIFFERENCE (P.d.)

- Is the workdone per unit charge in moving electric charge from one point to another in an electric field

OR

Is the difference in electrical potential between any two points.

Mathematically

$$\text{P.d.}(V) = \frac{\text{Workdone}}{\text{Charge}}$$

$$V = \frac{W}{q}$$

q

- The common SI unit of P.d. is VOLT (V)

## HOW ELECTRIC POTENTIAL IS CREATED

### Mechanism

- When electric charges move through a conductor an electric field is set up in the conductor
- This electric field interacts with electric charges and hence some energy is spent in moving the electric charge in the forward direction

## SIMPLE ELECTRIC CIRCUIT

- Is the circuit that consists of electronic equipment like source of moving charge (it may be battery/generator) connecting wire that is made of a conducting material (copper metal) and electrical device like;
- ⇒ Bulb, switches, or plug key, resistors, Ammeter, Voltmeter etc

### Electric circuit

Is a continuous conducting path between the terminal of the source of electricity such as cell or battery

### TYPES OF CIRCUIT

#### 01. Open electric circuit

Is a circuit in which flow of current stops because of open switch

#### Reason

Due to ~~closed~~ & open switch

#### 02. Closed electric circuit

Is the circuit in which current flows continuously

#### Reason.

→ Due to closed switch

## VOLTAGE

## HOW ELECTRIC POTENTIAL IS CREATED

### Mechanism

- When electric charges move through a conductor an electric field set up in the conductor
- This electric field interact with electric charges and hence some energy is spent in moving the electric charge in the forward direction

## SIMPLE ELECTRIC CIRCUIT

- Is the circuit that consist of electronic equipment like source of moving charge (it may be battery/generator) connecting wire that is made of a conducting material (copper metal) and electrical device like;
- ⇒ Bulb, switches or plug key, resistors, Ammeter, Voltmeter etc.

### Electric circuit

Is a continuous conducting path between the terminal of the source of electricity such as cell or battery

### TYPES OF CIRCUIT

#### 01. Open electric circuit

Is a circuit in which flow of current stops because of open switch

### Reason

Due to closed switch  
open

#### 02. Closed electric circuit

Is the circuit in which current flows continuously


### Reason:

→ Due to closed switch

## VOLTAGE


- ✓ it is measured by using a device known as VOLTMETER
- ✓ its SI-unit is VOLT(V)
- ✓ it is always connected parallel to the device when you want to measure its voltage drop across it.

CONSIDER.

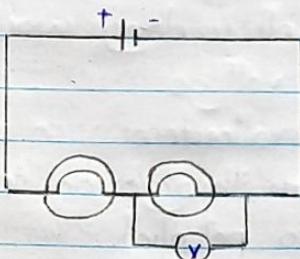


- ✓ Wrong connection of an ammeter can damage the circuit, so the red terminal of ammeter should be connected in series with the circuit

Consider

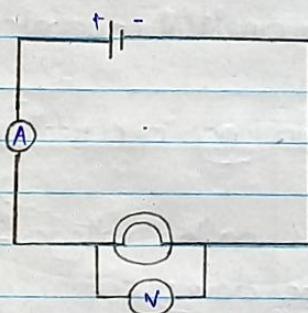

### SIMPLE CIRCUIT

Consider

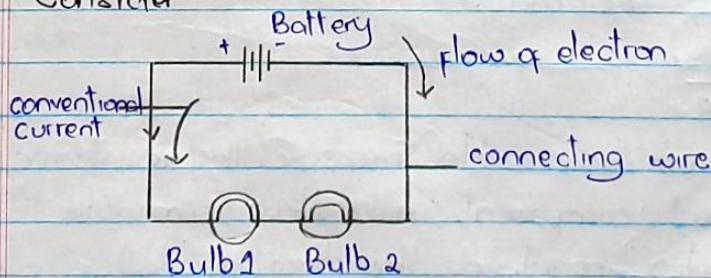

hints:

- ✓ Current always flows from positive to negative

- ✓ Electron always flow from negative to positive
- ✓ The potential difference is measured in volt

### ELECTROMOTIVE FORCE (EMF)

- ✓ Is the maximum potential difference between terminals of a cell when the cell is doing work
- ✓ It is also called voltage
- ✓ It is measured in voltmeter

It pumps current to flow through an electric circuit although it's not a force is just a potential.

- ✓ The difference between the electromotive force and the terminal voltage is known as lost volt

### RESISTANCE

#### Hints:

- ✓ As current flows through the circuit it encounters some opposing force.
- ✓ This force determines the flowing of current in a electric device
- ✓ Flowing of current depends on the voltage (pd) across the device and the nature of the device.
- ✓ The property of conductors that opposes the flow of electric charges depends on the relationship between the current and voltage across their ends.

### RESISTOR

- ✓ Is the device which is used to measure the resistance
- ✓ It is an electrical component with two terminals that is used to limit or regulate the flow of electric current in an electric circuit

## RESISTANCE

→ Is the measure of opposition of the flow of current in an electric circuit

Its SI-unit is ohm ( $\Omega$ )

## OHM ( $\Omega$ )

Is the resistance of a conductor in such a way that when a potential difference of 1 volt is applied to its ends with a current of 1 Ampere flows through it.

## TYPES OF RESISTORS

### Hints

They are divided according to the material used to make them and value of resistance offered.

Types of resistors due to materials used

#### 01 Wire wound resistor

⇒ It is made by winding wire made of a certain metallic alloys used to control amount of resistance

#### 02 Carbon resistor

⇒ Made by mixing carbon granules with varying amount of clay and moulding them into cylinders.

#### 03 Metal film resistor

⇒ Made of stable ceramic core created with metal alloys such as nickel, chromium

→ It is more accurate and more expensive than carbon resistor

#### 04 Metal oxide film resistor

⇒ Made up of a stable ceramic core coated with metal alloys such as Tin oxide

## TYPES OF RESISTORS DUE TO VALUE OFFERED

### 01 Fixed resistor

⇒ it has the value which cannot be changed e.g. 2Ω, 3Ω, 4Ω etc.

✓ Most carbon resistors are fixed resistor

### 02 Variable resistor

It has a resistor value which can be changed by means of control e.g. potentiometers, photo resistors and Rheostat.

#### RHEOSTAT

It is also called Variable resistance

✓ It is divided into two parts namely

##### 01 Known variable resistor


⇒ Involve the arrangement of number of known resistance which can be added or removed (Resistance box)

##### 02 Unknown variable resistor

⇒ its magnitude can be altered but its exact magnitude is not known.

## FACTORS AFFECTING RESISTANCE OF A WIRE

Consider

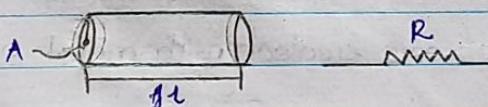

### 01 Length of a conductor

Length of a conductor varies direct proportional to the resistance of a wire

$$R \propto L - 01$$

⇒ As the length increase it lead to an increase in resistance

## 02 Temperature

Resistance varies direct proportion to the temperature  $^{\circ}\text{C}$

→ As the temperature increases it lead to the increase in resistance.

✓ For semi-conductors the increase in temperature cause the decrease in resistance.

## 03 Nature of material

Resistance depends on the type of material used for making conductor. e.g. Nichrome wire has more resistance than copper wire of the same dimensions.

→ Nichrome wire is used to heat element of electric fire

→ Copper is used mostly to connect wires

## 04 Cross-section area

Resistance of a wire varies inversely proportional to the cross section area

→ As the cross section area increase it tends to decrease resistance of a wire.

### GENERAL HINIS

Combine eqn 1 and eqn 2

$$R \propto l - 01$$

$$R \propto \frac{l}{A} - 02$$

$$R \propto l \cdot \frac{1}{A}$$

$$R \propto \frac{l}{A}$$

$$R = \frac{k \cdot l}{A}$$

$$k = AR_1$$

$k = \text{constant} = \text{Resistivity of material (G)}$

$$K = \frac{I}{A} = AR$$

$$\frac{I}{A} = R$$

$$= f = \frac{m^2 R}{l} = \Omega m.$$

$$\Omega \quad f = \Omega m.$$

## RESISTIVITY ( $\rho$ )

Is the ability of a material to oppose the flow of electric current

The SI-unit is ohm meter ( $\Omega m$ )

## CONDUCTANCE

- Is the reciprocal of resistance
- Its SI-unit is  $\frac{1}{\Omega m}$  or siemens ( $s$ )

$$G = \frac{1}{R}$$

## RESISTIVITY OF SOME MATERIALS AT 20°C

MATERIAL	RESISTIVITY ( $\Omega m$ )
Aluminium	$2.7 \times 10^{-8}$
Chromium	$1.3 \times 10^{-7}$
Copper	$1.68 \times 10^{-8}$
Iron	$9.7 \times 10^{-8}$
Lead	$2.1 \times 10^{-1}$
Silver	$1.6 \times 10^{-8}$
Constantan	$4.9 \times 10^{-7}$
Manganin	$4.8 \times 10^{-7}$
Nichrome	$1.0 \times 10^{-6}$
Glass	$1 \times 10^9 - 1 \times 10^{13}$
Rubber	$1 \times 10^{13} - 1 \times 10^{15}$
Quartz	$7.5 \times 10^{17}$

## OHM'S LAW

state that "At constant temperature a current flowing through a wire conductor is direct proportional to the potential difference across its ends."

Hints

$$V \propto I$$


$$V = kI$$

$k$  = constant = Resistance ( $R$ )

$$V = R I$$

$$\boxed{V = IR}$$

Graphically

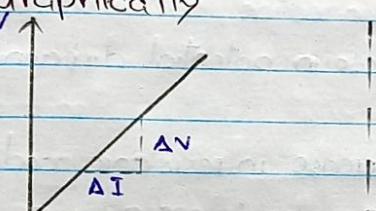

From the graph

$$\text{slope} = \frac{\Delta V}{\Delta I}, m = \frac{\Delta V}{\Delta I}$$

$$\Delta X \text{ with } \Delta Y$$


$m = \text{slope} = \text{resistance.}$

$$\boxed{R = \frac{\Delta V}{\Delta I}}$$

## VERIFICATION OF OHM'S LAW.


It can be verified by using Voltmeter ammeter method.

Consider the diagram.

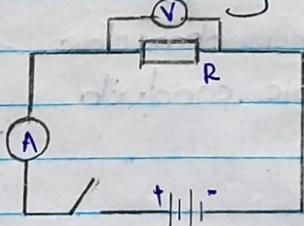

The graph is found to be straight

Pd(v)

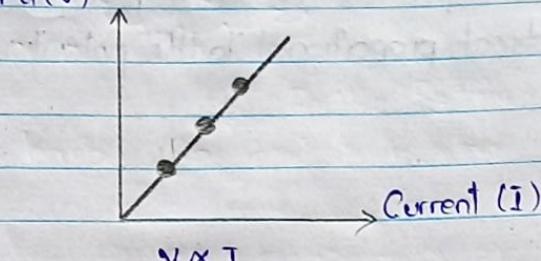

$$V = KI$$

$$V = RI$$

$$I = \frac{V}{R}$$

i.e. Current increase with increase in potential difference and vice versa


✓ Current increase with the decrease in resistance and vice versa

### OHMIC RESISTANCE

✓ The resistances that obey ohms law are said to have ohmic resistance. e.g. metallic alloys

its graph



V

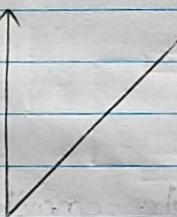

### NON-OHMIC RESISTANCE

✓ Resistances that do not obey ohms law  
e.g. electric valve and ionic conductor

graph

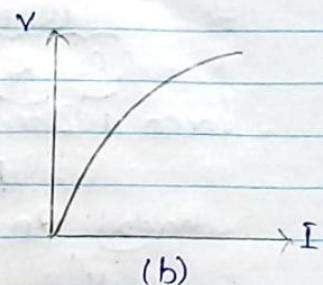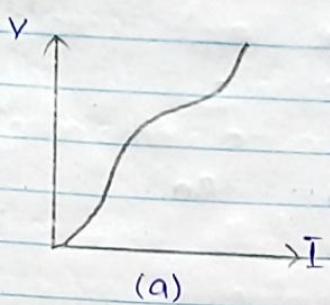

### LIMITATION OF OHM'S LAW


- 01 it does not apply to some electrolytes, e.g. dilute  $H_2SO_4$
- 02 it does not apply for conduction of electricity charges.
- 03 it does not hold in semiconductor (diode and transistors)

### COMBINATION OF RESISTORS

Resistors can be combined in series or in parallel form

#### SERIES ARRANGEMENT

Consider

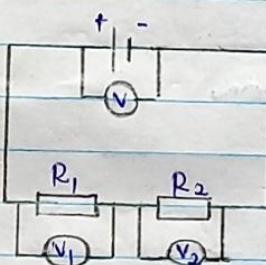

#### Conditions

01. P.d. across the battery = sum of p.d. around the conducting path
02. Current is the same at all points

#### Hints

Since p.d. is not the same then

$$V_T = V_1 + V_2$$

From ohms law  $V = IR$

$$V_T = IR_T, V_1 = IR_1, V_2 = IR_2$$

$$\therefore V_T = V_1 + V_2 \Rightarrow IR_T = IR_1 + IR_2$$

$$\pi R_1 = \pi (R_1 + R_2)$$

$$R_1 = R_1 + R_2$$

for n resistor.


$$R_T = R_1 + R_2 + R_3 + R_4 + \dots + R_n$$

whereby  $R_n$  is a last resistor

### CHARACTERISTICS OF RESISTANCE IN SERIES

01. The sum total of resistance in series increases with the increase in number of resistors.
02. The current tend to decrease as the number of resistors are increasing.  
⇒ (This explains that series connection of bulb are not brighter due to high resistance)
03. All elements (bulbs) in series circuit works simultaneously.  
⇒ This explains that if the circuit is broken anywhere between elements (bulbs) None of the element functions.

### PARALLEL CONNECTION

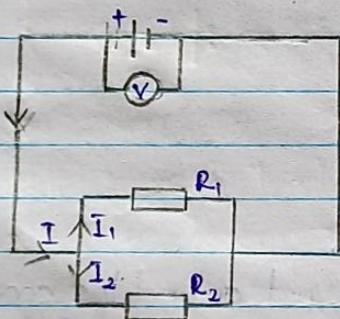

### Conditions

In parallel connection the current passing outside the branches is equal to the sum of the current in the individual branches.

$$\text{e.g. } I_T = I_1 + I_2$$

Voltage in each branch is the same

### Hints

Since the current is not the same then

$$I_T = I_1 + I_2$$

from ohms law  $V = IR$ ,  $I = V/R$

$$I_T = I_1 + I_2$$

$$I_T = \frac{V}{R_T}, I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}$$

from  $I_T = I_1 + I_2$

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$V \left( \frac{1}{R_T} \right) = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\left( \frac{1}{R_T} \right) = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

from (n) resistors

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Whereby  $R_n$  is the last resistance.

### CHARACTERISTICS OF RESISTANCE IN PARALLEL CONNECTION


- 01 Sum of resistance in parallel decreases with the increase in number of resistors
- 02 The current flowing in any resistor in parallel connection will be inversely proportional to the resistance.  
⇒ The more the resistance the less the resistance and viceversa
- ✓ This explains that arrangement of elements (bulbs) are brighter due to low effective resistance

- ⇒ Effective resistance (total resistance) decreases as the number of resistors keep increasing
- 03 Each resistor in parallel function independently with respect to the other resistor  
 ⇒ (This explains that if one bulb blow of the other bulbs will continue working)
- 04 Used in house wiring

### APPLICATION OF OHM'S LAW

01. it is applied in resistor network e.g series and parallel combination of resistors.
02. it is used to divide current (current divide theorem)

Consider

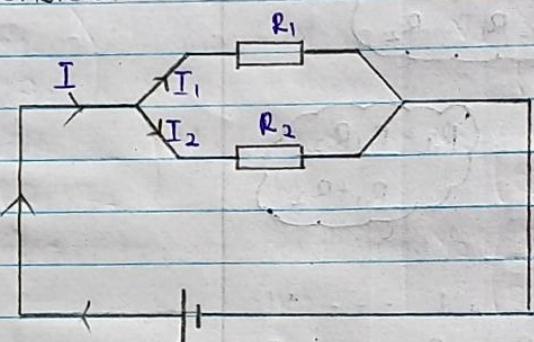

Hints 01

- The total current tend to be divided

$$\text{Effective resistance } R = \frac{R_1 R_2}{R_1 + R_2}$$

From ohms law

$$V = IR$$

$$I = \frac{V}{R}$$

Case 01

Current due to branch 1

$$I_1 = \frac{V}{R_1}$$

$$I_1 = V \left( \frac{1}{R} \right)$$

but

$$I_1 = IR \left( \frac{1}{R_1} \right)$$

But  $R = \text{Effective resistance}$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = I \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \left( \frac{1}{R} \right)$$

$$I_1 = I \left( \frac{R_2}{R_1 + R_2} \right)$$

$$I_1 = \frac{R_2}{R_2 + R_1}$$

CASE 02:

Current due to branch 2

$$I_2 = \frac{V}{R_2}$$

$$I_2 = V \left( \frac{1}{R_2} \right)$$

but  $V = IR$

$$I_2 = IR \left( \frac{1}{R_2} \right)$$

But  $R = \text{Effective resistance}$


$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_2 = I \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \left( \frac{1}{R_2} \right)$$

$$I_2 = I \left( \frac{R_1}{R_1 + R_2} \right)$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

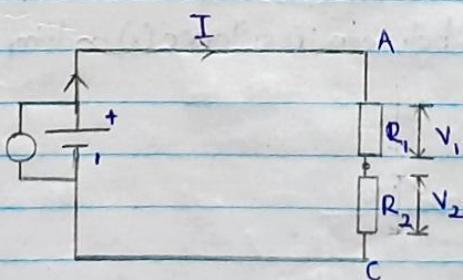3 kJh can used in dividing voltage (voltage divider theorem)  
Consider:



Hints

from ohms law

$$V = IR$$

But  $R = R_1 + R_2$  {effective resistance}

$$V = I(R_1 + R_2)$$

$$I = \frac{V}{R_1 + R_2}$$

Case 01

Voltage due to  $R_1$

$$V_1 = IR_1$$

$$\text{but } I = \frac{V}{R_1 + R_2}$$

$$V_1 = \left( \frac{V}{R_1 + R_2} \right) R_1$$

$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V$$

Case 02

Voltage due to  $R_2$

$$V_2 = IR_2$$

$$\text{but } I = \frac{V}{R_1 + R_2}$$

$$R_1 + R_2$$

$$V_2 = \left( \frac{V}{R_1 + R_2} \right) R_2$$

$$V_2 = \left( \frac{V}{R_1 + R_2} \right) R_2$$

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V$$

## INTERNAL RESISTANCE OF A CELL


Hints 01

Cell has an internal resistance that opposes the flow of electric current causes the potential drops across their resistance

The relationship between resistance ( $r$ ) and emf ( $E$ ) of a cell is given by

$$E = I(R + r)$$

Consider

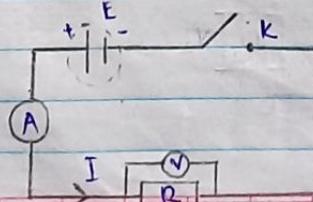

$$E = I(R + r)$$

Where  $E$  = Electromotive force

$I$  = Electric current

$r$  = Internal resistance

$R$  = External resistance (Load resistance)

P.d across  $R$  (terminal voltage),  $V = IR$

P.d across (Lost voltage)  $V_L = Ir$

$$E = IR + Ir$$

$$E = V_L + V$$

### Hint's 02

- 01 When the Terminal of the battery are short circuited when disconnected from their external circuit

⇒ The resistance of the circuit is the internal resistance of the cells.

✓ Recall from

$$E = I(R + r)$$

$$E = V + V_L$$

$$E = V + V_L \text{ Where } V = 0$$

$$E = V_L$$

$$E = Ir$$

- 02 The total emf available in the cell is used up in two way

✓ Driving the current through the cell to overcome internal resistance

✓ Driving the current through the external resistance  $R$

Recall,

✓ This eqn can be used to determine the internal resistance of a cell

✓ When the current  $I = 0$  then  $V = E$

## RESISTOR COLOUR CODES

Hints:

- ✓ Resistors which are used in determine devices always pointed with different colour texture called BAND
- ✓ The BAND represent the exactly value of a resistance it contains four band with different meaning

## RESISTOR's COLOUR CODES

Consider Table


	Colour	Code
Better	Black	0
Be	Brown	1
Ready	Red	2
Or	Orange	3
Your	Yellow	4
Great	Green	5
Big	Blue	6
Plan	Purple	7
Goes	Grey	8
Wrong	White	9

## TOLERANCE COLOUR CODES

- ✓ Colours of resistors may be represented in percentage
- Consider Table

Tolerance	$\pm 1\%$	$\pm 2\%$	$\pm 5\%$	$\pm 10\%$	$\pm 20\%$
Colour	Brown	Red	Gold	Silver	Nocolor

Consider the diagram

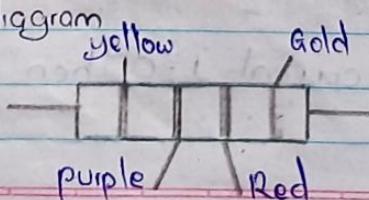

### Hints:

- ✓ First band represent the first digit
- ✓ Second band represent the second digit
- ✓ Third band (multiplier) represents the number of zero
- ✓ The fourth band (Tolerance) represent the percentage accuracy

Brown Black Green

Example: — 

Given the resistance above

find the value of the resistance

Solution

Bn	B1	Gn
1	0	5


1000000Ω

∴ The value of resistance is 1000000Ω

### WHEAT STONE BRIDGE METHOD

- ✓ Is an electrical bridge circuit used to measure the unknown resistance of a conductor

Consider

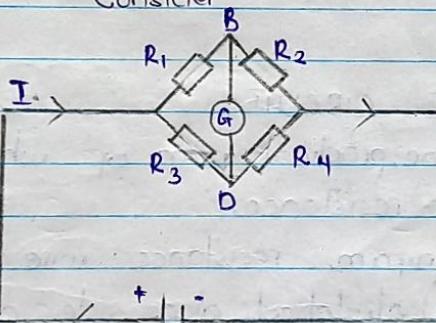

- ✓ The circuit above show that  $R_1$ ,  $R_2$  and  $R_4$  are known resistance and  $R_3$  is unknown
- ✓ The resistance  $R_4$  is varied until the balancing point is obtained where the galvanometer show no deflection

Hints o1

- ✓ At balancing point

$$V_{AB} = I_1 R_1, \quad V_{BC} = I_1 R_2$$

$$V_{AD} = I_2 R_3, \quad V_{DC} = I_2 R_4$$

## Hints 02

Potential at B and D are not equal.

## Reason

No current is flowing / passes through the galvanometer.  
So;

$$V_{AB} = V_{AD} \quad \text{and} \quad V_{BC} = V_{DC}$$

which means

$$\underline{V_{AB}} = \underline{V_{AD}}$$

$$V_{BC} \neq V_{DC}$$

$$\underline{X_1 R_1} = \underline{I_2 R_3}$$

$$\frac{I_1}{R_2} = \frac{I_2}{R_4}$$

$$\underline{R_1} = \underline{R_3}$$

$R_2$        $R_4$

## ADVANTAGES OF WHEATSTONE


- Measurement of resistance is not affected by internal resistance of the supply battery.
  - it is more sensitive when the resistance of four arms are nearly equal.

## MEIER BRIDGE CIRCUIT

- ✓ Is the one of the practical form of wheat stone bridge used for measuring resistance.
  - ✓ It consists of a uniform resistance wire let say AC (usually 100cm long) stretched along side a meter ruler
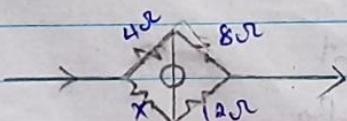
## Question.

The galvanometer in the bridge network shown in figure below, given no deflection what is like value of x.



## Solutions

$$R_1 = R_3$$

$$R_2 = R_4$$

$$\frac{4\Omega}{8\Omega} \times x = \frac{x}{12\Omega}$$


$$\frac{8\Omega}{8\Omega} \times x = \frac{4\Omega \times 12\Omega}{8\Omega}$$

$$x = 6\Omega$$

$$x = 6\Omega$$

$$\therefore x = 6\Omega, R_3 = 6\Omega$$

Consider

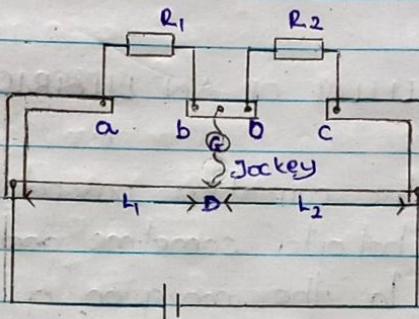

Hints

- ✓ Resistance  $R_1$  is connected across the gap ab
- ✓ Another resistor  $R_2$  is connected across the gap bc
- ✓ As the jockey is moved along the AC at one position let say D, the galvanometer will read zero
- ✓ The meter bridge is then said to be balanced
- ✓ D is the balancing point
- ✓  $R_x$  is the resistance to be measured

Consider from figure

$$R_1 \times L_1 = 01$$

$$R_2 \times L_2 = 02$$

$$L_1 + L_2 = 100\text{cm} = 03$$

$$R_1 = K L_1 = 04$$

$$R_2 = K L_2 = 05$$

Take eqn 04 and 05 then  
divide

$$\frac{R_1}{R_2} = \frac{L_1}{KL_2}$$

$$R_2 = \frac{KL_2}{R_1}$$

$$\frac{R_1}{R_2} = \frac{L_1}{L_2}$$

— 06

Recall from eqn 03

$$L_1 + L_2 = 100\text{cm}$$

Make  $L_2$  the subject formula  
 $L_2 = (100\text{cm} - L_1)$

Recall eqn 06

$$\frac{R_1}{R_2} = \frac{L_1}{L_2}$$

$$R_2 = \frac{L_2}{L_1} R_1$$

$$\frac{R_1}{R_2} = \frac{L_1}{(100 - L_1)}$$

— 07

## HEATING EFFECT OF AN ELECTRIC CURRENT

Hints:

- When an electric current is passed through a conductor become hot after sometime and produce heat
- This happens due to the conversion of some electric charges energy passing through the conductor into heat e.g. the steel wool stand will get hot as current flows through the circuit.
- Here electrical energy is converted to heat energy in the steel wool.

## FACTORS AFFECTING HEAT QUANTITY

01 Resistance of a conductor

- The higher the heat the resistance and vice versa

02 Magnitude of the electric current

- The higher the current the more the heat produced.

03 The time for which current flow

The heat produced by an electric current is proportional to the time taken by the current to pass through a conductor

### JOULE'S LAW

Hints

It tell us the relationship between resistance, current and heat generated

Joule's law state that "When an electric current is passed through a conductor the heat evolved in a given time is directly proportional to the resistance of the conductor in ohms multiplied by the square of the current in Amperes"

HINTS

$$H \propto I^2 R t$$

$$H = K I^2 R t$$

K: Constant

$$(H = I^2 R t) \rightarrow 01$$

Recall from ohm's law

$$V = IR$$

$$R = \frac{V}{I}$$

$$H = I^2 \left( \frac{V}{I} \right) t$$

$$H = I V t$$

$$(H = I V t) \rightarrow 02$$

GENERAL HINTS

The workdone become transferred to molecular energy in the conductor accompanied by rise in temp °C

Recall from potential difference in term of workdone

$$P.d(V) = \frac{w \cdot d}{q}$$

$$V = \frac{w}{q}$$

$$(V = \frac{w}{q}) \rightarrow 03$$

from

$$I = \frac{q}{t}$$

$$\therefore V = \frac{w}{q} = It$$

$$\therefore W = (It)V$$

$$(W.d = ItV) \rightarrow 04$$

Recall eqn 03

$$W = qV$$

$$\text{but } V = IR$$

$$W = qIR$$

$$(W = IqR) \rightarrow 05$$

- ✓ This energy is given out in form of heat
- $$w.d = H = itv = I^2 R t$$

### ELECTRIC POWER

- ✓ Is the rate at which electrical energy is converted to other forms of energy e.g. heat, light
- Hints.

Electric power = Electrical energy / time

Δ Electrical energy = work done = Heat energy

P = Energy

time

$$P = I^2 R t$$

t

$$(P = I^2 R) \text{ --- 06}$$

from ohms law

$$V = IR$$

Recall from eqn 06

$$P = I^2 R$$

$$P = I (IR)$$

$$(P = IV) \text{ --- 07}$$

Recall again from eqn 06

$$P = I^2 R$$

from ohms law

$$V = IR, I = \frac{V}{R}$$

$$P = \left( \frac{V}{R} \right)^2 R$$

$$P = \frac{V^2}{R^2} R$$

$$(P = \frac{V^2}{R}) \text{ --- 08}$$

### KILOWATT HOUR (KWH)

Is the energy supplied by the rate of working of 1000 watts for 1 hour

Hints

1 kilowatt hour = 1000 watt hour

= 1000  $\frac{W}{s}$  for 1 hour

=  $1000 \frac{W}{s} \times (60 \times 60) s$

$$1000 \text{ J} \times 3600 = 3600000 \text{ J}$$
$$3.6 \times 10^6 \text{ J}$$

The energy given in (1kwh) is  $3.6 \times 10^6 \text{ J}$   
Commercial unit of electrical energy is (kwh)

### EFFICIENCY OF ELECTRIC DEVICE

Is the ratio of useful output power to the input power expressed in percentage

Mathematically

$$\text{Efficiency} = \frac{\text{Useful output power}}{\text{Input power}} \times 100\%$$

### APPLICATION OF HEATING EFFECT

- Used in electrical heating appliance such as iron room heater water heater
- Used in electric bulb to produce light
- Used in electric fuse

NB: The wire used in the filament of household bulb should have high resistance and high melting point (heated to a very high temp°C) in order to emit light.

### MEASUREMENT OF ELECTRICAL POWER AND BILLING OF ELECTRICAL ENERGY

- Used in electrical heating appliance such as
- Power is the rate of doing work.

OR

Is the workdone per unit time in (second)

- Power companies like TANESCO usually measure the electrical energy in kilowatt hour (kwh)

Hint 01:

$$1 \text{ kWh} = 1 \text{ kW} \times 1 \text{ hour}$$
$$= (1000 \text{ W} \times 60 \times 60)$$

$$1 \text{ kWh} = 3600000 \text{ J}$$

$$1 \text{ kWh} = 3600 \text{ kJ}$$

Hint 02:

High voltage is used for commercial transmission of electrical energy

Reason:

- ✓ Inorder to reduce the power loss during electrical transmission.

### ELECTRICAL APPLIANCES

- ✓ Is the device that uses heating element to produce heat energy
- ✓ Nichrome wire is among of the heating element due to high melting point
- ✓ The common electrical appliances include heaters, electric iron, bulbs, kettles, cookers, fridges, television and air conditioners

### RATING OF THE ELECTRICAL APPLIANCES

( Is the device that uses heating element to produce heat energy.) Out of concept

- ✓ Is the rate at which the appliance dissipate energy  
Each electrical appliances has its own rating which enables us to know energy dissipated  
e.g.
- ✓ An appliance marked 3000W, 240V dissipates energy at the rate of 3000 Joules per second when

connected to 240V

The resistance of filament increases with the increase in temp<sup>o</sup>C

### POWER RATINGS OF COMMON ELECTRICAL APPLIANCES.

Electrical appliance	Power rating at 240V
Immersion water	2000W (2kW)
Electrical heater	2000W (2kW)
Electrical Iron	1000W (1kW)
Electrical kettle	1500W (2.5kW)
Colour TV	300W
Refrigerator	120W
Light bulb	25W - 150

Hints:

✓ If the main supply falls below 240V, the rating of the appliances would drop

Similarly when the power supply rises, the rating would rise and it would damage the appliance due to over heating

### ELECTRICAL INSTALLATION OF A HOUSE

Hints:

Domestic electricity is supplied by two cables

⇒ Live (L)

⇒ Neutral (N)

✓ The third cable is Earth (E) that is used to provide extra safety

LIVE CABLE (L)

✓ It is 240V relative to the neutral

- ✓ it is represented by BROWN and RED colour  
Then potential difference the LIVE and NEUTRAL wire is  $240V - 0V = 240V$

### NEUTRAL CABLE (N)

- ✓ It is earthed at the power station  
Reason.

$\Rightarrow$  To ensure current at neutral remains zero potential ( $V=0V$ ) so it cannot give an electric shock on touching

- ✓ it is represented by BLUE or BLACK colour

### EARTH CABLE (E)

It is introduced to provide extra safety especially in electrical appliance

- ✓ it is represented by YELLOW or GREEN colour


### THREE PIN PLUG

- ✓ it consists of all three cables which are live cable, neutral cable and earth cable

Hints:

- ✓ A fuse is connected to LIVE cable

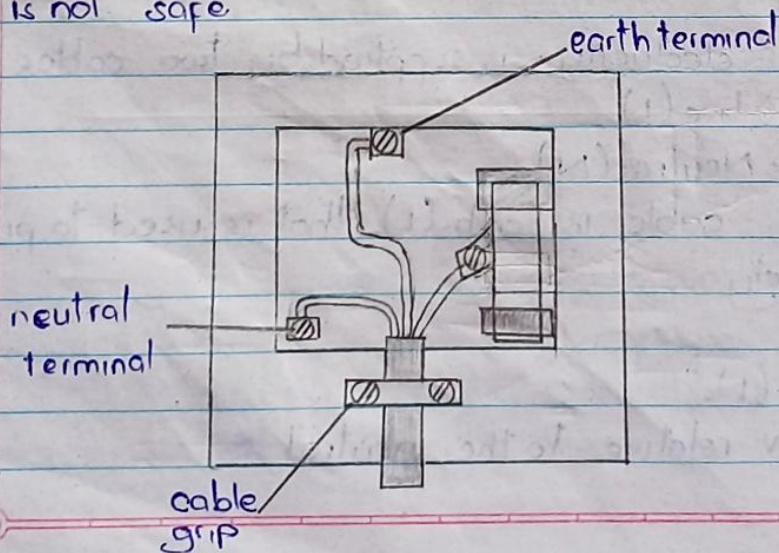Sometime a fuse can be connected to neutral which is not safe



N.B

- ✓ The earth pin/cable is longer than the other two
- ✓ Switch must be off when you push the plug into the socket

### TWO PIN PLUG

- ✓ It consists of only two cables which is live cable and neutral cable
- ✓ An appliance using two-pin plug its body is not connected to the earth

### FUSE

- ✓ Is a safety device used to protect an electric circuit against excess current

OR

- ✓ Is a short piece of special wire which melt when more than a rated amount of current passes through it.
- ✓ It is made of a thin copper wire covered with tin or a lead-tin alloy.
- ✓ It works as a circuit breaker or stabilizer which protects the device from damage.

### Types of fuse:

- a) Rewireble fuse
- b) Cartridge fuse

### MECHANISM OF A FUSE

- ✓ A fuse works on the principle of heating effect of an electric current.
- ✓ It is always connected in series with the electrical circuit to protect from over current in the running cable.
- ✓ When the excessive current flows in the circuit, the fuse

it opens (breaks) the circuit

- the excessive flow may lead to the break down of wire and stop the flow of current  
then the fuse can be replaced with the new one with suitable rating

#### APPLICABLE OF FUSE

- Electrical appliances (devices)
- Auto mobiles such as car, trucks, and other vehicles
- Spanners, portable electronics, hard disc drivers
- Fuses in capacitors, transformers etc.


#### WHAT HAPPEN IF WE DONT USE FUSE

- If we don't use fuses, electrical faults occurs in the wiring and it burns the wire and electrical appliances and this may start fire at home

Also the lives of television, computers, radios and other home appliances may put at risk.

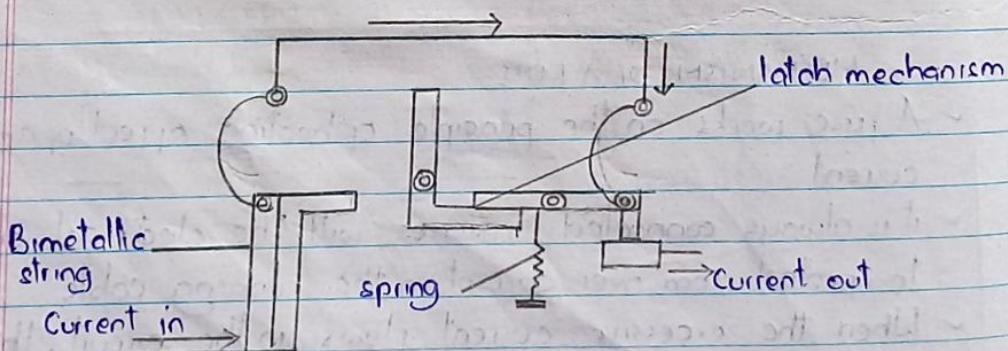
#### CIRCUIT BREAKER

- Is a type of switch that cut off the flow of current when the current exceeds a specific volume.


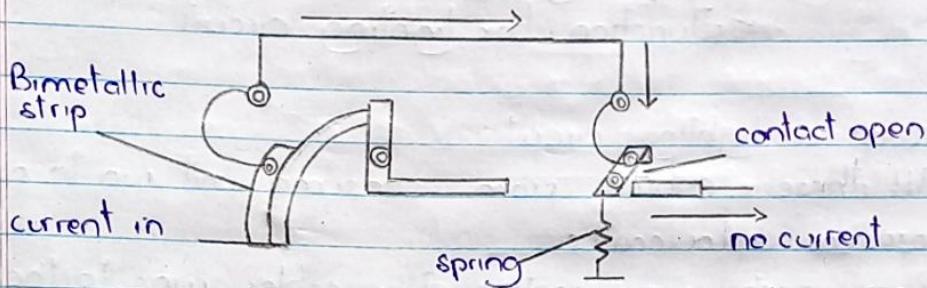
## MECHANISM OF CIRCUIT BREAKER

When the current exceed tend to increase the temperature and bimetallic strip bend to push latch mechanism which enable the spring to cut off the current.



## DOMESTIC WIRING CIRCUIT

- ✓ The power company connects power to the house up the consumers unit where they wiring starts.
- ✓ Consumer unit is the place where the main switch, main fuse and distribution board and placed in a single box or unit.
- ✓ From the consumer unit the cables branch into the various parts of the house

## TYPES OF DOMESTIC WIRING CIRCUIT

01. Ring main circuit
02. Lightning circuit

## RING MAIN CIRCUIT

- ⇒ It is the cable which begins and ends at the consumer unit
- ✓ its three cables are forming ring around part of the house
- ✓ its fuse is of 30A fuse.

## LIGHTING CIRCUIT

In this circuit the first lamp connected from the consumer unit in turn is connected to the second lamp and so on.

### TYPES OF LIGHTING CIRCUIT

- ✓ loop in lighting circuit
- ✓ Junction box lighting circuit

#### Loop in lighting circuit

- ✓ All these cables from consumer unit run to each roses one after another.

From each rose another set of cables runs to the switch which operates the light.

#### Junction Box lighting circuit

All three cables from consumer unit run to one junction box to another where one cable runs to the light and another run to the switch for that light.

### REPAIRING ELECTRICAL APPLIANCES FAULTS

- ✓ (All three cables from consumer unit run to one junction). incorrect.
- ✓ Multimeter and live mains lead indicator are devices important when checking electrical appliances faults.

### LIVE MAIN LEAD INDICATOR (TESTOR)

- ✓ Is the electronic device used for testing the flow of electric current

### Multimeter

Is the single meter for measuring current both (a.c and d.c)

## REPAIRING OF FAULTS PROCEDURES

If electrical appliance fail to work, the following procedure should be done

- 01 Check by using live mains lead indicator if there is power or not.
- 02 Check the cable from the socket to the appliance.
- 03 If no faults is detected open the plug and then check the fuse.
- 04 Check each cable for continuity by using multimeter.
- 05 If the cables are working properly check the fault is in the element by using a multimeter.
- 06 If element is in fault replace element as repair.
- 07 If the element is not in fault, look for loose connection.

## SOURCES OF FAULTS IN DOMESTIC SYSTEM

- 01 When fuse blows/melts
- 02 Wire cutting
- 03 Wire joining
- 04 Socket getting dusty
- 05 Switches breaking

## CELL

A cell is a device used to cause a flow of current electric in a conductor

### Types of Electrochemical cells:

01. Primary cells.

02. Secondary cells.

## PRIMARY CELLS

- Is a cell which produces current as a result of irreversible

chemical changes taking place within a cell  
it is a cell that is designed to be used once and discarded.

it cannot be recharged after being used.

✓ Primary cells have high density and get discharged slowly

Examples of primary cells.

01. Simple cell

02. Leclanché cell


03. Dry cell

#### CHARACTERISTICS OF PRIMARY CELL

- ✓ Have high energy density and slow in discharge and easy to use
- ✓ There are no fluids in the cell hence it is also called dry cell
- ✓ It has high internal resistance
- ✓ It has an irreversible chemical reaction
- ✓ Its design is smaller and lighter
- ✓ Its initial cost is cheap

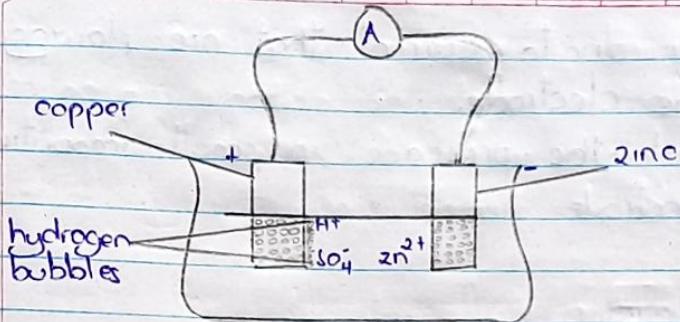
#### SIMPLE CELL

- Is a device that converts chemical energy into electrical energy
- It consists of two electrodes (two different metals) and an electrolyte solution.
- It is made from copper as anode, zinc as a cathode and dilute acid as electrolyte.



The processes that occur when the cell is in operation

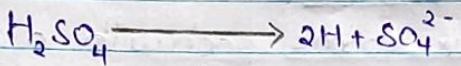- ✓ oil  $H_2SO_4$  separates into sulphate ions ( $SO_4^{2-}$ ) and hydrogen ion ( $H^+$ )



At Anode

Zinc metal dissolved into solution to form zinc cation which reacts with sulphate anion to form zinc sulphate

$$Zn^{2+} + SO_4^{2-} \longrightarrow ZnSO_4$$

At cathode

Hydrogen cation discharges to liberate hydrogen gas (bubbles)



#### DEFECTS OF A SIMPLE CELL

Simple cell has two defects which causes the current to drop quickly when the cell is being used.

These are

01. Local action
02. Polarization.

#### LOCAL ACTION

Local action of a battery is the deterioration of the battery

of the battery due to current that are flowing from and the same electrode.

→ it is caused the presence of small impurities in the zinc electrode.


### Exercise

1. An electric cooker has coil resistance  $50\Omega$ . If it operated on  $240V$  main supply for 1 hour how much energy does it produce?
2. A house has six rooms each with a  $85W$ ,  $240V$  bulb. If the bulbs are switched on 06:50pm to 10:30pm determine the power consumed by bulbs per day.
3. A bulb rated  $120V$ ,  $75W$  burns continuously for 3 days. Given that the cost of one unit ( $1kW$ ) is  $320$  Tsh determine the:
  - a) Total electrical energy consumed
  - b) Total power bill.

### LECLANCHÉ' CELL

- It is a cell that is made of carbon as an anode, zinc as cathode, ammonium chloride ( $\text{NH}_4\text{Cl}$ ) solution and depolarizer manganese dioxide ( $\text{MnO}_2$ )

Diagram

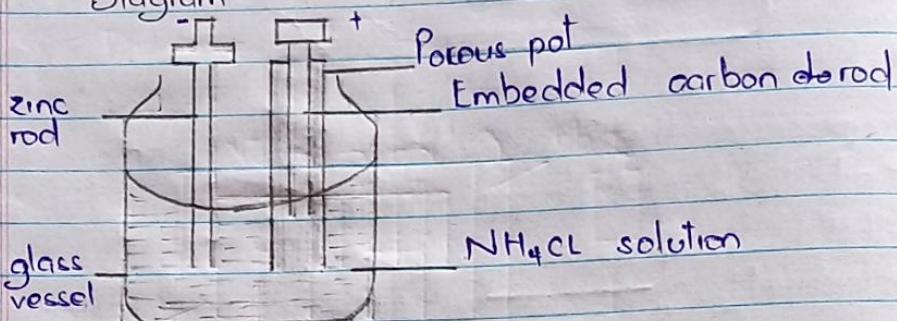


### DRY CELL

- Is a modified Leclanché cell in which ammonium chloride solution is replaced with ammonium chloride jelly.

### FUNCTION OF $\text{MnO}_2$

- It acts as a depolarizer
- Ammonium chloride ( $\text{NH}_4\text{Cl}$ ) and zinc chloride acts as an electrolyte

Diagram.

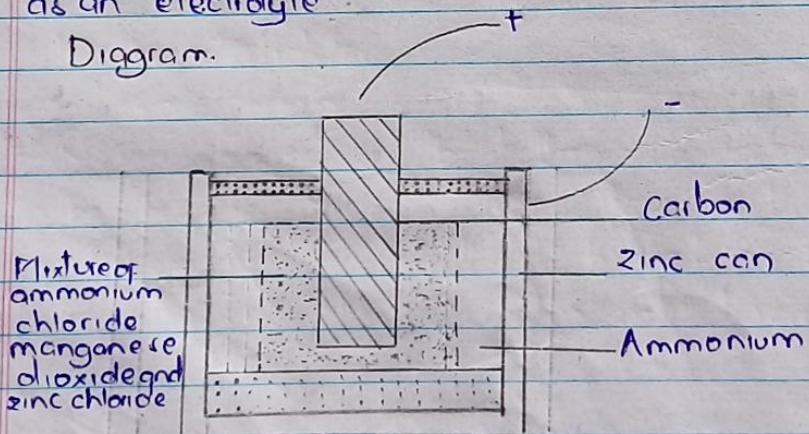

### USES OF DRY CELL

- Used to operate on radar, electronic calculator and other small electrical devices

### ADVANTAGES OF DRY CELL

- ✓ it is portable
- ✓ The chemicals for its production are relatively cheap
- ✓ it has a relatively high emf.
- ✓ it is able to recover from its polarized.

### DISADVANTAGES OF DRY CELL

- ✓ It cannot be recharged thus disposed after use.

### SECONDARY CELLS

- ✓ Are cells which can be recharged after running down.  
e.g. lead acid cells and Nickel ferrous cells.
- ✓ They are also called ACCUMULATORS

### ADVANTAGES OF SECONDARY CELL

- ✓ last stronger than primary cells.
- ✓ Can supply large current (low internal resistance) for a long time.
- ✓ Can be recharged.


### DISADVANTAGES OF SECONDARY CELL

- ✓ Heavy and cumbersome to carry.
- ✓ The electrolyte is corrosive.
- ✓ it produces gases which may explode if ignited.
- ✓ it cannot produce large current in cold weathers (lowering the temperature causes chemical reactions to proceed more slowly)
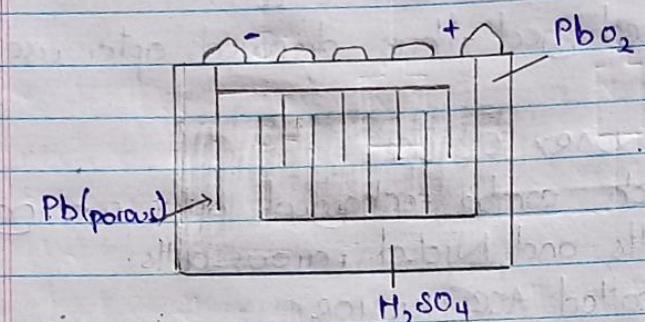
### LEAD ACID BATTERY

- ✓ It consists of two plates of Lead immersed in water dilute sulphuric acid.

- ⇒ These are anode of lead (IV) oxide and cathode of spongy lead.
  - An electrolyte is separated by insulator called separator
  - Cathode joining together to form negative terminal while anode joining together to form positive terminal
- Diagram.



### DISCHARGING OF LEAD-ACID BATTERY

Discharging

Means that

- A battery tends to provide electrical energy

Charging of lead-acid battery

Charging

- ✓ Its aim is to drive off the acid out of plates and return it to the electrolyte
- ✓ During charging
- ⇒ Negative terminal of the battery charger is connected to the negative terminal of the battery and vice versa
- ✓ When battery is fully discharged, the battery is said to be sulphated (will not function until it is recharged)

### TAKING CARE OF ACCUMULATORS

- ✓ Cells should be charged regularly and should never be left discharged

- ✓ the acid level should be maintained by adding distilled water when necessary (never add acid)
- ✓ the terminal should be kept clean and greased.
- ✓ Rough handling should be avoided
- ✓ The cell should not be short circuit e.g. if you connect two terminals to each other rate.
- The rate specified by manufacturer should not be exceeded during charging.

#### USES OF ACCUMULATORS.

- To provide power in motor vehicles.
- To provide energy to power domestic appliances such as radio.
- ✓ Used together with solar panels to convert solar energy to electrical energy
- They are used to store electrical energy


#### ARRANGEMENT OF CELLS

##### O1. SERIES ARRANGEMENT

Hints.

- In this arrangement the positive terminal of one cell is connected to the negative terminal of another cell
- Electrical current is the same to each cell.
- ✓ Total voltage across the cell is equal to the sum of voltage arrangement.


Diagram.

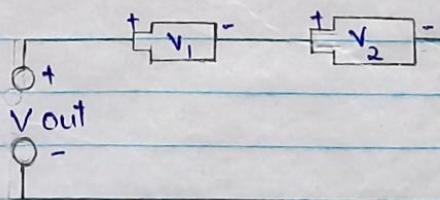

## Parallel arrangement

- In parallel arrangement all the positive Terminal of the cells are connected together and negative terminal of the cells are connected together.

## Diagram

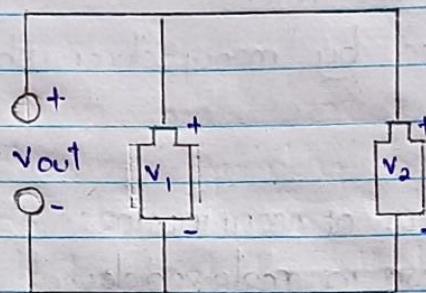

## Hints.

- ✓ Total voltage of all the cells is the same as that of single cell
  - ✓ Currents is not the same